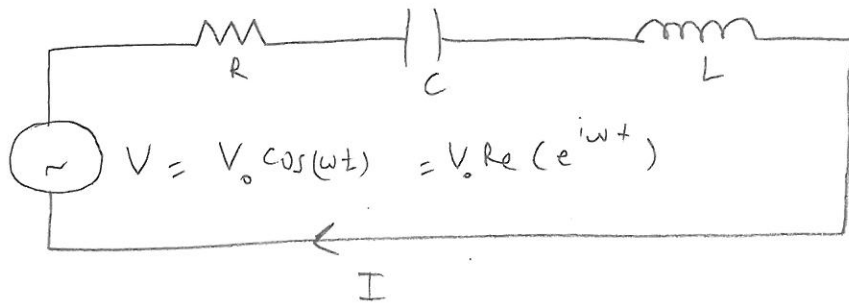


Week 11

Micro teaching : AC circuits



Individual impedance :

Re	Re + Im
R	R
$1/\omega C$	$(-i/\omega C) e^{-i\pi/2}$
ωL	$(i\omega L) e^{i\pi/2}$

Total impedance : $R + i\omega L - \frac{i}{\omega C} = Z$

$$\sqrt{R^2 + \omega^2 L^2 + \frac{1}{\omega^2 C^2}} = \operatorname{Re}(Z)$$

1. Let $(L=0)$

$$V_R = \frac{R}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} V_0 \cos(\omega t)$$

$$V_C = \frac{1/\omega C \cdot V_0 \cos(\omega t - \frac{\pi}{2})}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

Lags by $\pi/2$

2. Let $(C=0)$ Task

$$V_R = ? = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t)$$


$$V_C = ? = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \frac{\pi}{2})$$

In an RC circuit:


HP / LP filter

Task

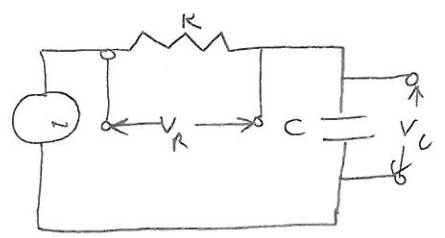1. Notice constant $I(\omega t)$ doesn't pass through C




In:

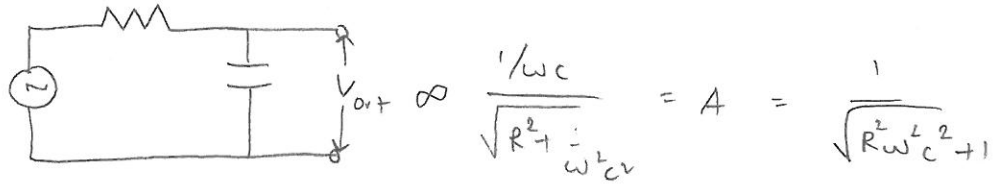

$$\Rightarrow |V_{out}| = V_0 A \Rightarrow \text{Low pass } (\omega \rightarrow 0) \Rightarrow (A=1)$$

2. Notice all $I(\omega t)$ passes through R

In:

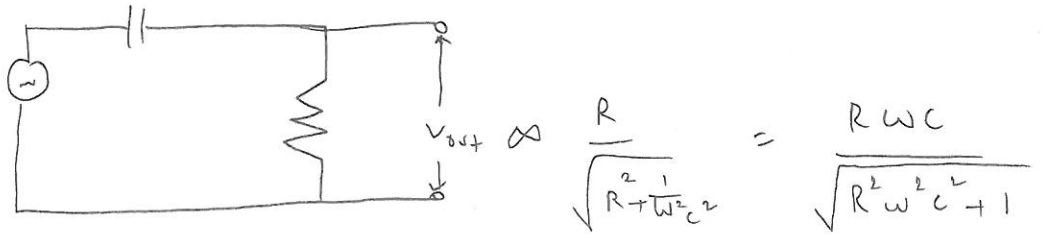


$$\Rightarrow |V_{out}| = V_0 A \Rightarrow \text{High pass}$$

$$(\omega \rightarrow \infty) \Rightarrow A=1$$

$$\Rightarrow V_C \Rightarrow \text{LP}$$

$$V_R \Rightarrow \text{HP}$$

1.

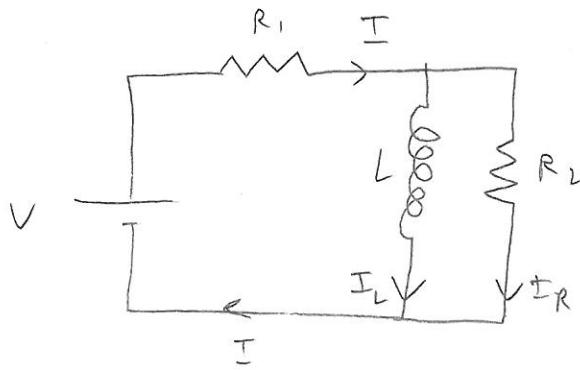

a. * $I = I_L + I_R$; $V - IR_1 - L \dot{I}_L = 0$

$$\dot{I}_L - I_R R_2 = 0$$


$$V - IR_1 - I_R R_2 = 0$$

*' \Rightarrow Calc. $I_L(t)$ & $I_R(t)$ using $I_L(0) = 0$
 $I_L(\infty) = \frac{V}{R_1}$

* Calc. $\int_0^{\infty} I_R(t) R_2 dt = ?$

b. hint: what energy is stored in $-L' = \frac{1}{2} L I_L^2(\infty)$

2.

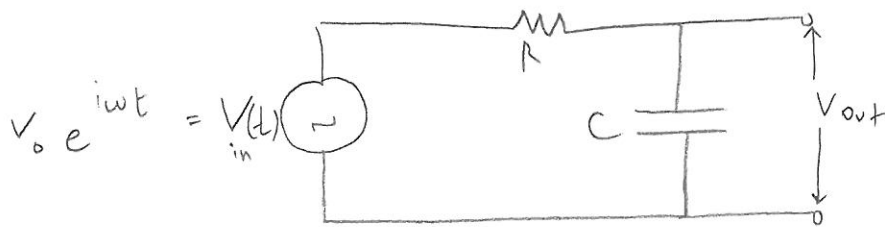

$$Z = R - \frac{i}{\omega C}$$

a. $I(t) = \frac{V_{in}}{Z}$

b. $V_{out} = \frac{Z_c}{Z} V_{in}(t)$

c. Easy way: $I = \frac{Z_c V_{in}(t)}{Z_r} = \frac{\frac{1}{\omega C} V_{in}}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} = \frac{V_{in}}{\sqrt{1 + R^2 \omega^2 C^2}}$

$\tan \phi = \frac{\text{Im}(Z_c / Z)}{\text{Re}(Z_c / Z)}$

; complex part only useful for phase info.

d. e. Not a big change.

3. a. $\vec{B} = ?$ obtain \vec{E} from: $\vec{\nabla} \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$

Should have same phase info.

b. $T \sim [0, 2\pi]$

$(kx - \omega t) \rightarrow$ do not complicate things


c. $P = \frac{2}{c} \langle S \rangle$ assuming photons bounce off elastically.

$\vec{F} = \vec{A} \cdot P$

4. a. $\vec{E} = -\frac{V}{d} (1 - e^{-\frac{t}{RC}}) \hat{z}$

according to Ampere's Law: $\vec{\nabla} \times \vec{B} = \mu_0 J = 0$?

Maxwell correction: $\vec{\nabla} \times \vec{B} = \mu_0 (J + \epsilon_0 \frac{\partial \vec{E}}{\partial t})$
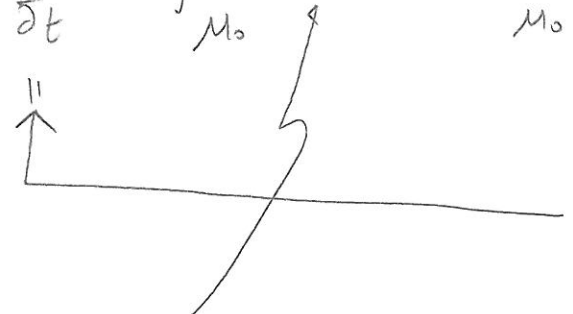
$$\frac{I}{dc} = \int \mathbf{J}_{\text{disp. current}} \cdot d\mathbf{s} = \int \epsilon_0 \frac{\partial \mathbf{E}}{\partial t} \cdot d\mathbf{s} = \int \frac{1}{\mu_0} \nabla \times \mathbf{B} \cdot d\mathbf{s} = \frac{1}{\mu_0} \int \mathbf{B} \cdot d\mathbf{l}$$


$\frac{2\pi r B}{\mu_0}$

because of \times product \hat{z} : \vec{B} cannot have direction of $\hat{z} \Rightarrow \hat{\phi}$

b. $\vec{J} = \frac{1}{\mu_0} (\vec{E} \times \vec{B})$

c. Express \vec{J} in terms of $V_c = v_0 (1 - e^{-\frac{t}{RC}})$

then
$$\omega = \int dt \left(\int_{r=R_0} \mathbf{J}(t) \cdot d\mathbf{s} \right)$$

5. $I(-\frac{d}{2}, t) = I(\frac{d}{2}, t) = 0 \Rightarrow I ?$ linear in z
time part $\cos(\omega t)$

eq. of continuity: $\frac{d\lambda}{dt} + \frac{dI}{dz} = 0 \Rightarrow$ obtain $\lambda(z, t)$

$$P(t) = \int_{-d/2}^{d/2} z \lambda(t) dz = ?$$

then calc.
$$\langle P \rangle = \frac{\omega^2 \mu_0}{12\pi \epsilon_0 c^3}$$